



INSTITUTO POLITÉCNICO NACIONAL
ESCUELA SUPERIOR DE CÓMPUTO



U.A: Arquitectura de Computadoras

“Práctica 11: Cartas ASM”

Grupo: 3CV11

Profesor: Vega García Nayeli

Sánchez Becerra Ernesto Daniel

Unidad de Control

Código de implementación

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity unidad_control is
    Port ( ini : in STD_LOGIC;
          clr : in STD_LOGIC;
          clk : in STD_LOGIC;
          a0 : in STD_LOGIC;
          z : in STD_LOGIC;
          la : out STD_LOGIC;
          ea : out STD_LOGIC;
          lb : out STD_LOGIC;
          ec : out STD_LOGIC;
          eb : out STD_LOGIC);
end unidad_control;

architecture Behavioral of unidad_control is

    type estados is (e0,e1,e2);
    signal actual,siguiente : estados;

    begin

        process(clk, clr)
        begin
            if (clr = '1') then
                actual <= e0;
            elsif (rising_edge(clk)) then
                actual <= siguiente;
            end if;
        end process;

        process(actual,ini,z,a0)
        begin
            la <= '0';
            lb <= '0';
            ea <= '0';
            eb <= '0';
            ec <= '0';

            case actual is
                when e0 =>
                    lb <= '1';
                    if (ini = '1') then
                        siguiente <= e1;
                    else
                        la <= '1';
                        siguiente <= e0;
                    end if;
                when e1 =>
                    ea <= '1';
                    if (z = '1') then -- arreglo igual a cero
                        siguiente <= e2;
                    else -- arreglo diferente de cero
                        if (a0 = '1') then
                            eb <= '1';
                            siguiente <= e1;
                        else
                            siguiente <= e1;
                        end if;
                    end if;
                when e2 =>
                    ec <= '1';
                    if (ini = '1') then
                        siguiente <= e2;
                    else
                        siguiente <= e0;
                    end if;
            end case;
        end process;

    end Behavioral;
```

Código de simulación

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb_unidad_control is
end tb_unidad_control;

architecture Behavioral of tb_unidad_control is
    component unidad_control
    Port ( ini : in STD_LOGIC;
          clr : in STD_LOGIC;
          clk : in STD_LOGIC;
          a0 : in STD_LOGIC;
          z : in STD_LOGIC;
          la : out STD_LOGIC;
          ea : out STD_LOGIC;
          lb : out STD_LOGIC;
          ec : out STD_LOGIC;
          eb : out STD_LOGIC);
    end component;
    -- input signs
    signal ini, clk, clr, a0, z : STD_LOGIC;

    -- output signs
    signal la, lb, ea, eb, ec : STD_LOGIC;

    -- Clock period
    constant clk_period : time := 10ns;


begin
    -- Instantiate
    UC : unidad_control Port map (
        ini => ini,
        clr => clr,
        clk => clk,
        a0 => a0,
        z => z,
        la => la,
        ea => ea,
        lb => lb,
        ec => ec,
        eb => eb
    );

    -- Clock process
    CLOCK : process
    begin
        clk <= '0';
        wait for clk_period/2;
        clk <= '1';
        wait for clk_period/2;
    end process;


    -- process stimuli
    SP : process
    begin
        clr <= '1';
        wait for 30 ns;
        clr <= '0';
        wait for 60 ns;
        ini <= '1';
        wait for 10 ns;
        ini <= '0';
        wait for 50 ns;
        a0 <= '1';
        wait for 20 ns;
        a0 <= '0';
        wait for 20 ns;
        a0 <= '1';
        wait for 10 ns;
        a0 <= '0';
        wait for 120 ns;
        z <= '1';
        wait;
    end process;

end Behavioral;
```

Diagrama RTL

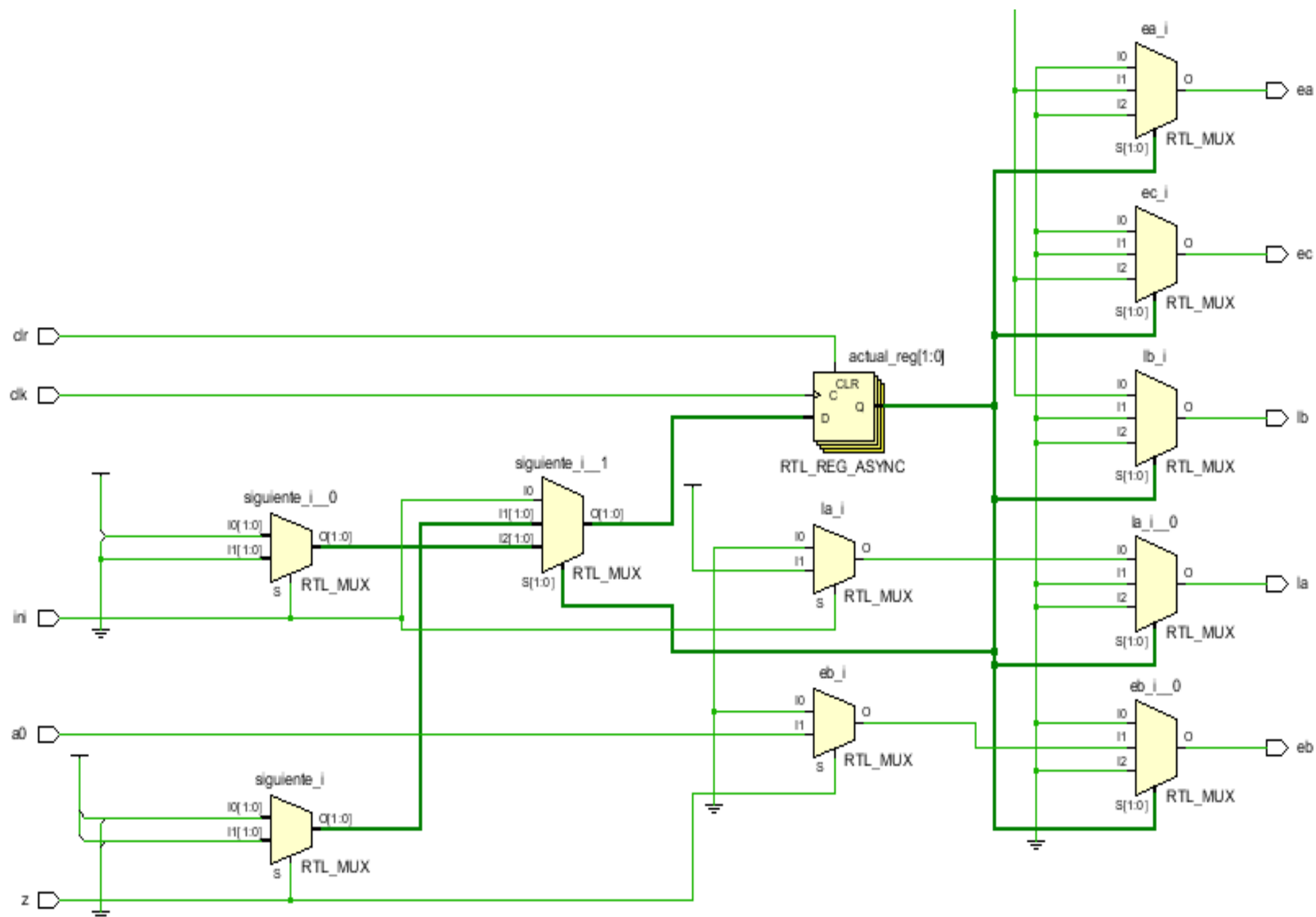

Forma de onda

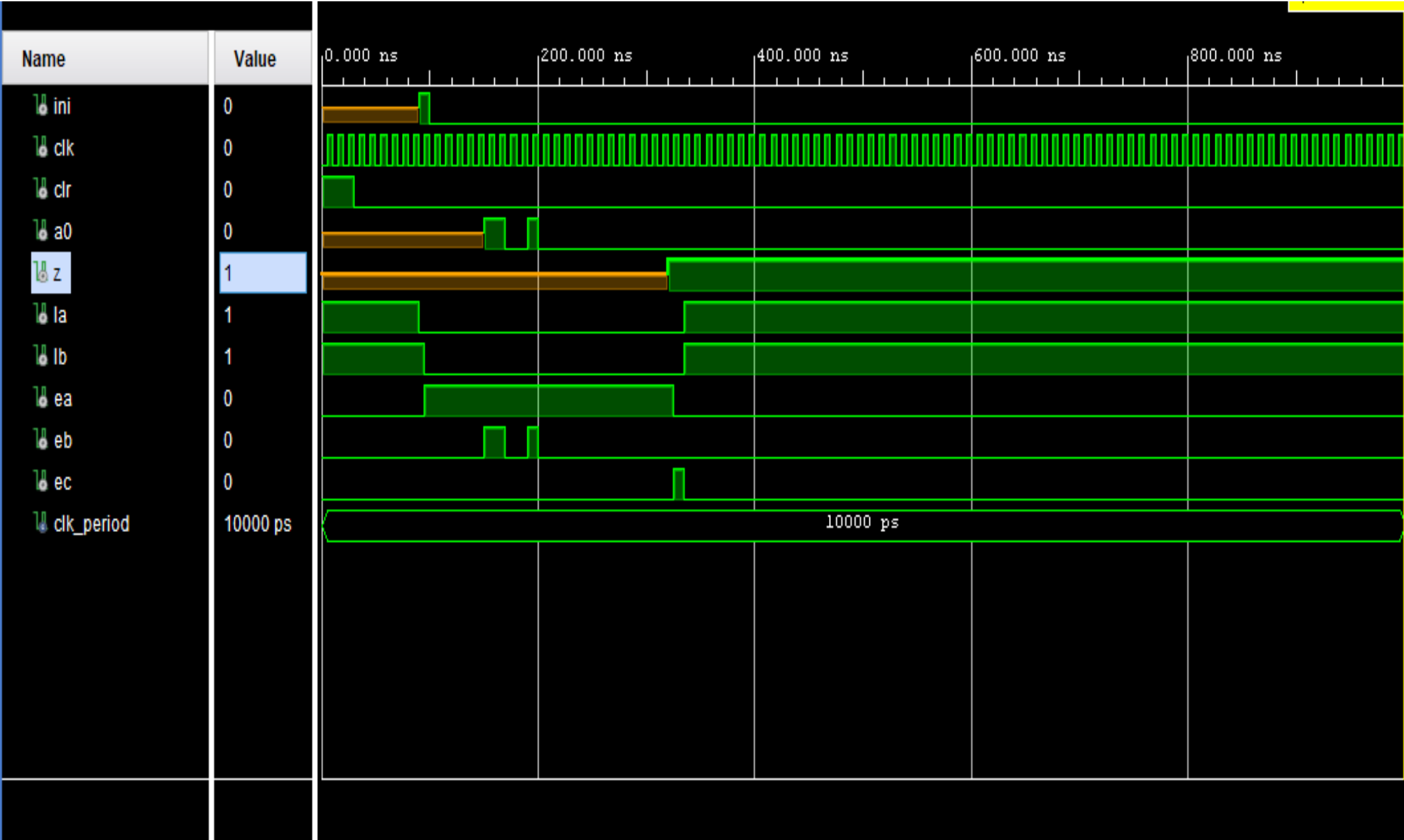

Contador

Código de implementación

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Contador is
    Port ( lb : in STD_LOGIC;
          eb : in STD_LOGIC;
          clr : in STD_LOGIC;
          clk : in STD_LOGIC;
          qb : out STD_LOGIC_VECTOR (3 downto 0));
end Contador;

architecture Behavioral of Contador is
    constant zero: std_logic_vector(3 downto 0) := "0000";
    begin
        process(clk, clr, eb, lb)
            variable aux_qb : STD_LOGIC_VECTOR(3 downto 0);
            begin
                if (clr = '1') then
                    aux_qb := zero;
                elsif (rising_edge(clk)) then
                    if (lb='1' and eb='1') then
                        aux_qb := aux_qb;
                    elsif (lb='1' and eb='0') then
                        aux_qb := zero;
                    elsif (lb='0' and eb='1') then
                        aux_qb := aux_qb + 1;
                    end if;
                end if;

                qb <= aux_qb;
            end process;
        end Behavioral;
```

Código de simulación

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb_Contador is
end tb_Contador;

architecture Behavioral of tb_Contador is
    component Contador is
        Port ( lb : in STD_LOGIC;
              eb : in STD_LOGIC;
              clr : in STD_LOGIC;
              clk : in STD_LOGIC;
              qb : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    -- input signs
    signal lb, eb, clr, clk : STD_LOGIC;

    -- output signs
    signal qb : STD_LOGIC_VECTOR(3 downto 0);

    begin

        -- Instaciate component for test
        COUNT : Contador Port map(
            lb => lb,
            eb => eb,
            clr => clr,
            clk => clk,
            qb => qb
        );

        -- Clock process
        CLOCK : process
        begin
            clk <= '0';
            wait for 5ns;
            clk <= '1';
            wait for 5ns;
        end process;

        -- Stimulus process
        SP : process
        begin
            clr <= '1';
            lb <= '0';
            eb <= '0';
            wait for 150 ns;


            clr <= '0';
            eb <= '1';
            wait for 150 ns;

            eb <= '0';
            lb <= '1';
            wait for 150 ns;


            wait;
        end process;

    end Behavioral;
```

Diagrama RTL

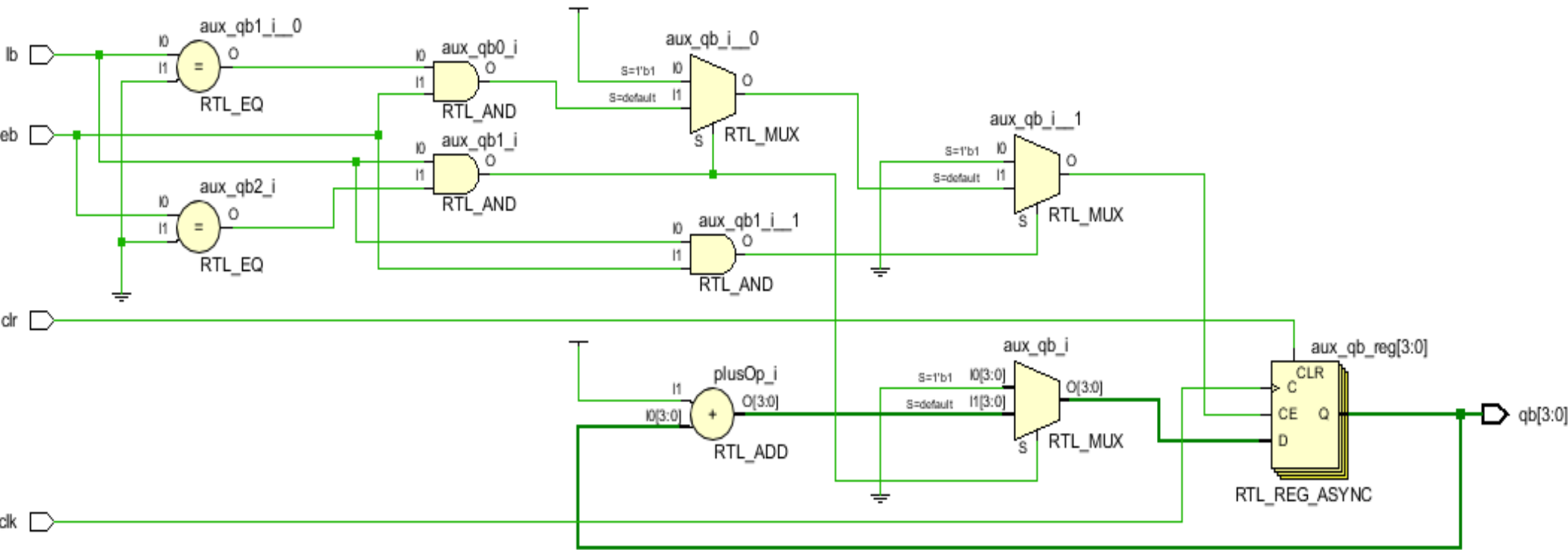

Forma de onda

 

Arreglo

Código de implementación

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Registro is
    Port ( la : in STD_LOGIC;
          ea : in STD_LOGIC;
          clk : in STD_LOGIC;
          clr : in STD_LOGIC;
          da : in STD_LOGIC_VECTOR (8 downto 0);
          qa : out STD_LOGIC_VECTOR (8 downto 0));
end Registro;

architecture Behavioral of Registro is
    signal aux_a : STD_LOGIC_VECTOR(8 downto 0); -- bus
begin

    process(clk,clr,la,ea)
    begin
        if (clr = '1') then
            aux_a <= "000000000";
        elsif(rising_edge(clk)) then
            if (la = '0' and ea = '0') then
                aux_a <= aux_a;
            elsif (la = '1' and ea = '0') then
                aux_a <= da;
            elsif (la = '0' and ea = '1') then
                aux_a <= to_stdlogicvector(to_bitvector(aux_a) SRL 1);
            end if;
        end if;
    end process;
    qa <= aux_a;
end Behavioral;
```

Código de simulación

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb_Registro is
end tb_Registro;

architecture Behavioral of tb_Registro is
    component Registro is
        Port ( la : in STD_LOGIC;
              ea : in STD_LOGIC;
              clk : in STD_LOGIC;
              clr : in STD_LOGIC;
              da : in STD_LOGIC_VECTOR (8 downto 0);
              qa : out STD_LOGIC_VECTOR (8 downto 0));
    end component;

    -- input signs
    signal la, ea, clk, clr : STD_LOGIC;
    signal da : STD_LOGIC_VECTOR(8 downto 0);

    -- output signs
    signal qa : STD_LOGIC_VECTOR(8 downto 0);

    -- clock period definition
    constant clk_period : time := 10 ns;

begin


    -- Instaciate component
    REG : Registro Port map(
        la => la,
        ea => ea,
        clk => clk,
        clr => clr,
        da => da,
        qa => qa
    );

    -- clock process
    CLOCK : process
    begin
        clk <= '0';
        wait for clk_period/2;
        clk <= '1';
        wait for clk_period/2;
    end process;


    -- Stimulus process
    SP : process
    begin
        da <= "110011001";
        wait for 150 ns;
        clr <= '0';
        la <= '1';
        ea <= '0';
        wait for 150 ns;
        la <= '0';
        ea <= '1';
        wait for 150 ns;

        wait;
    end process;
end Behavioral;
```

Diagrama RTL

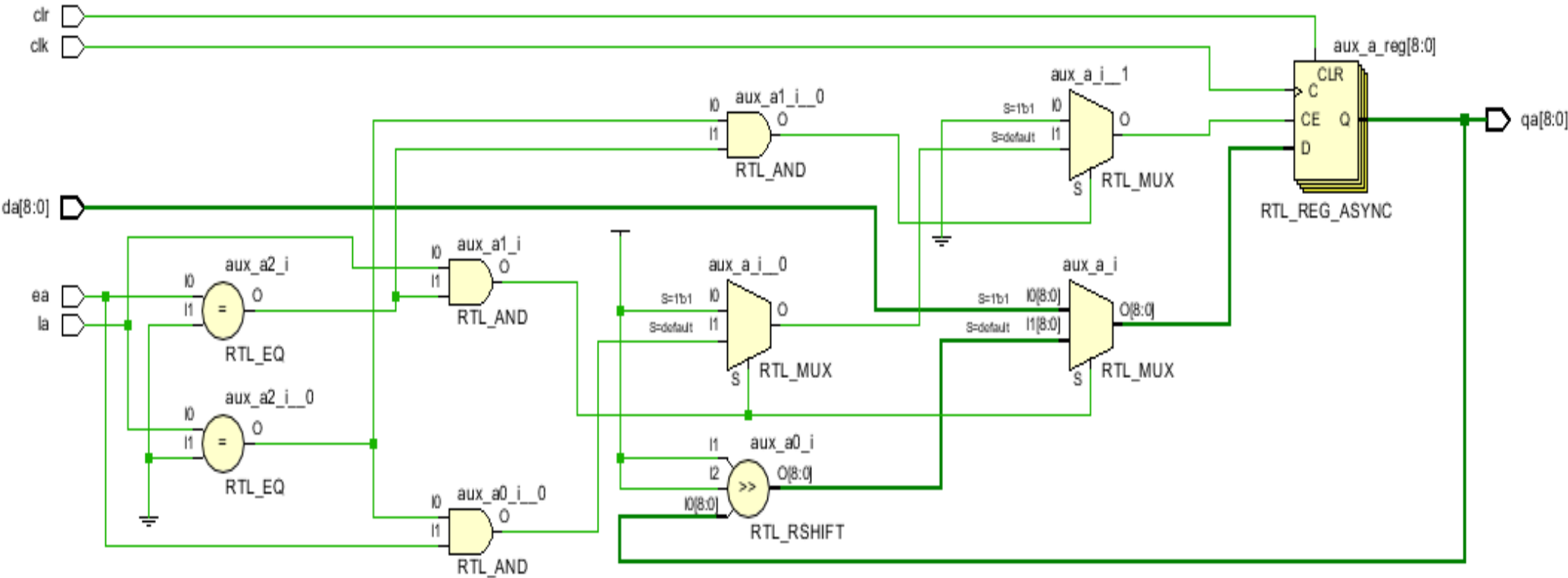

Forma de onda

 

Decodificador

Código de implementación

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Decodificador is
    Port ( qb : in STD_LOGIC_VECTOR (3 downto 0);
          digito_out : out STD_LOGIC_VECTOR (6 downto 0));
end Decodificador;

architecture Behavioral of Decodificador is -- "gfedcba"
    constant digito_0 : STD_LOGIC_VECTOR(6 downto 0) := "0111111";
    constant digito_1 : STD_LOGIC_VECTOR(6 downto 0) := "0000110";
    constant digito_2 : STD_LOGIC_VECTOR(6 downto 0) := "1011011";
    constant digito_3 : STD_LOGIC_VECTOR(6 downto 0) := "1001111";
    constant digito_4 : STD_LOGIC_VECTOR(6 downto 0) := "1100110";
    constant digito_5 : STD_LOGIC_VECTOR(6 downto 0) := "1101101";
    constant digito_6 : STD_LOGIC_VECTOR(6 downto 0) := "1111101";
    constant digito_7 : STD_LOGIC_VECTOR(6 downto 0) := "0000111";
    constant digito_8 : STD_LOGIC_VECTOR(6 downto 0) := "1111111";
    constant digito_9 : STD_LOGIC_VECTOR(6 downto 0) := "1101111";

    begin
        process(qb)
            begin
                case qb is
                    when "0000" => digito_out <= digito_0;
                    when "0001" => digito_out <= digito_1;
                    when "0010" => digito_out <= digito_2;
                    when "0011" => digito_out <= digito_3;
                    when "0100" => digito_out <= digito_4;
                    when "0101" => digito_out <= digito_5;
                    when "0110" => digito_out <= digito_6;
                    when "0111" => digito_out <= digito_7;
                    when "1000" => digito_out <= digito_8;
                    when OTHERS => digito_out <= digito_9;
                end case;
            end process;
        end Behavioral;
```

Código de simulación

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb_Decodificador is
end tb_Decodificador;

architecture Behavioral of tb_Decodificador is
    component Decodificador is
        Port ( qb : in STD_LOGIC_VECTOR (3 downto 0);
              digito_out : out STD_LOGIC_VECTOR (6 downto 0));
    end component;

    -- input signal
    signal qb : STD_LOGIC_VECTOR (3 downto 0);

    -- output signal
    signal digito_out : STD_LOGIC_VECTOR (6 downto 0);

    begin


        -- Instantiate component
        DECO : Decodificador Port map(
            qb => qb,
            digito_out => digito_out
        );

        -- Stimulus process
        SP : process
        begin
            -- Vamos a probar con cada numero
            qb <= "0000"; -- 0
            wait for 10 ns;
            qb <= "0001"; -- 1
            wait for 10 ns;
            qb <= "0010"; -- 2
            wait for 10 ns;
            qb <= "0011"; -- 3
            wait for 10 ns;
            qb <= "0100"; -- 4
            wait for 10 ns;
            qb <= "0101"; -- 5
            wait for 10 ns;
            qb <= "0110"; -- 6
            wait for 10 ns;
            qb <= "0111"; -- 7
            wait for 10 ns;
            qb <= "1000"; -- 8
            wait for 10 ns;
            qb <= "1001"; -- 9


            wait;
        end process;

    end Behavioral;
```

Diagrama RTL

 

Forma de onda

 

Multiplexor

Código de implementación

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Multiplexor is
    Port ( digito_in : in STD_LOGIC_VECTOR (6 downto 0);
          ec : in STD_LOGIC;
          digito_final : out STD_LOGIC_VECTOR (6 downto 0));
end Multiplexor;

architecture Behavioral of Multiplexor is
    constant guion : STD_LOGIC_VECTOR(6 downto 0) := "1000000"; -- gfedcba
    begin
        with ec select
            digito_final <= digito_in when '1',
            guion when others;
    end Behavioral;
```

Código de simulación

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb_Multiplexor is
end tb_Multiplexor;

architecture Behavioral of tb_Multiplexor is
    component Multiplexor
        Port ( digito_in : in STD_LOGIC_VECTOR (6 downto 0);
              ec : in STD_LOGIC;
              digito_final : out STD_LOGIC_VECTOR (6 downto 0));
    end component;

    -- input signs
    signal digito_in : STD_LOGIC_VECTOR(6 downto 0);
    signal ec : STD_LOGIC;

    -- output sign
    signal digito_final : STD_LOGIC_VECTOR(6 downto 0);


    begin

        -- Instantiate component
        MUX : Multiplexor Port map(
            digito_in => digito_in,
            ec => ec,
            digito_final => digito_final
        );


        -- Stimulus process
        SP : process
        begin
            ec <= '0';
            wait for 20 ns;

            ec <= '1';
            digito_in <= "0111111"; -- 0
            wait for 20 ns;
            digito_in <= "0000110"; -- 1
            wait for 20 ns;
            digito_in <= "1011011"; -- 2
            wait for 20 ns;
            digito_in <= "1001111"; -- 3
            wait for 20 ns;
            digito_in <= "1100110"; -- 4
            wait for 20 ns;
            ec <= '0';
            wait for 20 ns;
            ec <= '1';
            wait for 20 ns;
            digito_in <= "1101101"; -- 5
            wait for 20 ns;
            digito_in <= "1111101"; -- 6
            wait for 20 ns;
            digito_in <= "0000111"; -- 7
            wait for 20 ns;
            digito_in <= "1111111"; -- 8
            wait for 20 ns;
            digito_in <= "1100111"; -- 9
            wait for 20 ns;
            ec <= '0';
            wait for 20 ns;
            wait;
        end process;
    end Behavioral;
```

Diagrama RTL

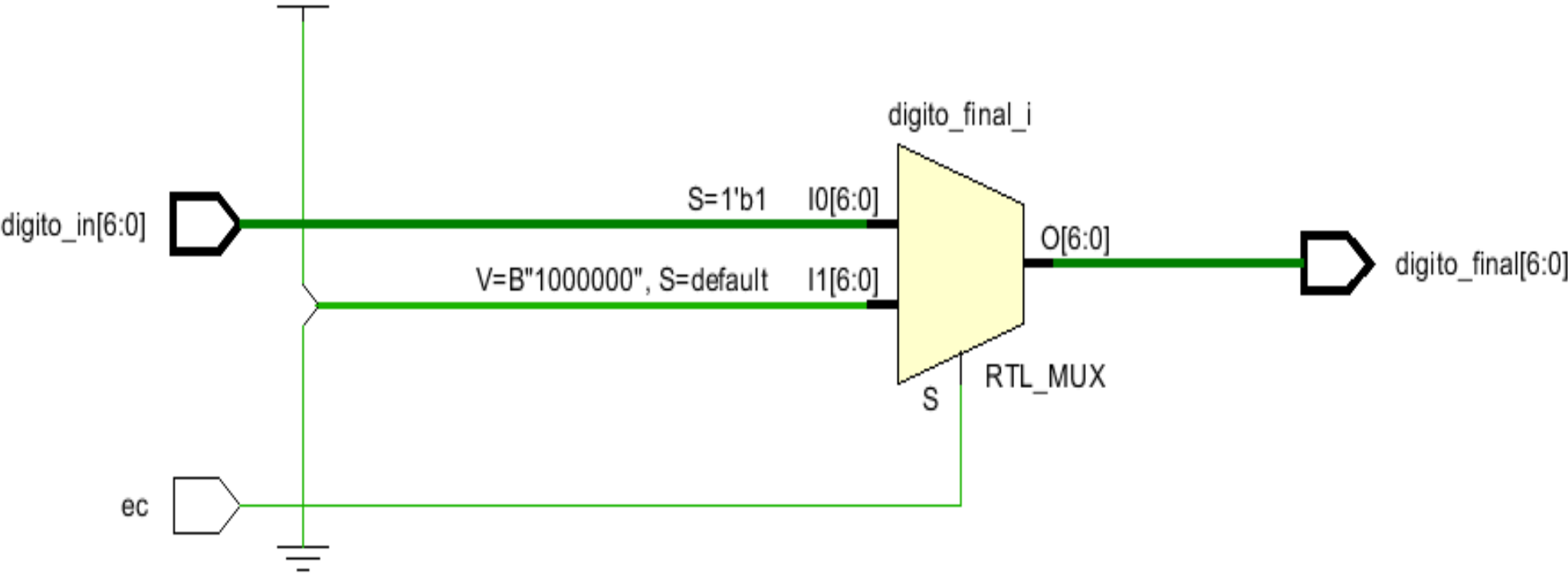

Forma de onda

 

Arquitectura Completa

Código de implementación

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity cartaASM is
    Port ( clr : in STD_LOGIC;
          clk : in STD_LOGIC;
          ini : in STD_LOGIC;
          data_in : in STD_LOGIC_VECTOR (8 downto 0);
          data_out : out STD_LOGIC_VECTOR (8 downto 0);
          digit_out : out STD_LOGIC_VECTOR (6 downto 0));
end cartaASM;

architecture Behavioral of cartaASM is
    -- unidad de control
    component unidad_control is
        Port ( ini, clr, clk, a0, z : in STD_LOGIC;
              la, ea, lb, ec, eb : out STD_LOGIC);
    end component;

    -- registros
    component Registro is
        Port ( la, ea, clk, clr : in STD_LOGIC;
              da : in STD_LOGIC_VECTOR (8 downto 0);
              qa : out STD_LOGIC_VECTOR (8 downto 0));
    end component;

    -- contador
    component Contador is
        Port ( lb, eb, clr, clk : in STD_LOGIC;
              qb : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    -- decodificador
    component Decodificador is
        Port ( qb : in STD_LOGIC_VECTOR (3 downto 0);
              digito_out : out STD_LOGIC_VECTOR (6 downto 0));
    end component;

    -- multiplexor
    component Multiplexor is
        Port ( digito_in : in STD_LOGIC_VECTOR (6 downto 0);
              ec : in STD_LOGIC;
              digito_final : out STD_LOGIC_VECTOR (6 downto 0));
    end component;
```

```

-- señales o buses de alambrado
signal sgnLA, sgnLB, sgnEA, sgnEB, sgnEC, sgnZ : STD_LOGIC;
signal sgnOutCounter : STD_LOGIC_VECTOR(3 downto 0);
signal sgnOutDeco : STD_LOGIC_VECTOR(6 downto 0);
signal sgnData : STD_LOGIC_VECTOR(8 downto 0);

begin

sgnZ <= '1' when sgnData = "000000000" else '0';
-- Instanciar modulo de unidad de control
UC : unidad_control
    Port map(
        ini => ini,
        clr => clr,
        clk => clk,
        a0 => sgnData(0),
        z => sgnZ,
        la => sgnLA,
        ea => sgnEA,
        lb => sgnLB,
        ec => sgnEC,
        eb => sgnEB
    );

-- Instanciar modulo de registro
REG : Registro
    Port map(
        la => sgnLA,
        ea => sgnEA,
        clk => clk,
        clr => clr,
        da => data_in,
        qa => sgnData
    );

-- Instanciar modulo de contador
CONT : Contador
    Port map(
        lb => sgnLB,
        eb => sgnEB,
        clr => clr,
        clk => clk,
        qb => sgnOutCounter
    );

-- Instanciar modulo de decodificacion
DECO : Decodificador
    Port map(
        qb => sgnOutCounter,
        digito_out => sgnOutDeco
    );

-- Instanciar modulo de multiplexor
MUX : Multiplexor
    Port map(
        digito_in => sgnOutDeco,
        ec => sgnEC,
        digito_final => digit_out
    );

data_out <= sgnData;

end Behavioral;

```

Código de simulación

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb_asm is
end tb_asm;

architecture Behavioral of tb_asm is

    component cartaASM
    Port ( clr : in STD_LOGIC;
          clk : in STD_LOGIC;
          ini : in STD_LOGIC;
          data_in : in STD_LOGIC_VECTOR (8 downto 0);
          data_out : out STD_LOGIC_VECTOR (8 downto 0);
          digit_out : out STD_LOGIC_VECTOR (6 downto 0));
    end component;

    -- input signs
    signal ini : STD_LOGIC;
    signal clk : STD_LOGIC;
    signal clr : STD_LOGIC;
    signal data_in : STD_LOGIC_VECTOR (8 downto 0);

    -- output signs
    signal data_out : STD_LOGIC_VECTOR (8 downto 0);
    signal digit_out : STD_LOGIC_VECTOR (6 downto 0);

    constant clk_period : time := 10 ns;

begin

    -- clock
    CLOCK_P : process
    begin
        clk <= '0';
        wait for clk_period/2;
        clk <= '1';
        wait for clk_period/2;
    end process;

    uut : cartaASM Port map(
        clr => clr,
        clk => clk,
        ini => ini,
        data_in => data_in,
        data_out => data_out,
        digit_out => digit_out
    );
```



```

-- Process stimulus
process_stimuli : process
begin

    clr <= '1';
    clr <= '0';
    wait for 20ns;
    data_in <= "101101011";
    wait for 20 ns;
    ini <= '1';
    wait for 150 ns;

    ini <= '0';
    clr <= '1';
    wait for 20 ns;
    clr <= '0';
    data_in <= "000011101";
    wait for 20 ns;
    ini <= '1';
    wait for 150 ns;

    ini <= '0';
    clr <= '1';
    wait for 20 ns;
    clr <= '0';
    data_in <= "000010000";
    wait for 20 ns;
    ini <= '1';
    wait for 150 ns;


    ini <= '0';
    clr <= '1';
    wait for 20 ns;
    clr <= '0';
    data_in <= "100001000";
    wait for 20 ns;
    ini <= '1';
    wait for 150 ns;

    ini <= '0';
    clr <= '1';
    wait for 20 ns;
    clr <= '0';
    data_in <= "000000000";
    wait for 20 ns;
    ini <= '1';
    wait for 150 ns;


    wait;
end process;
end Behavioral;

```


Diagrama RTL

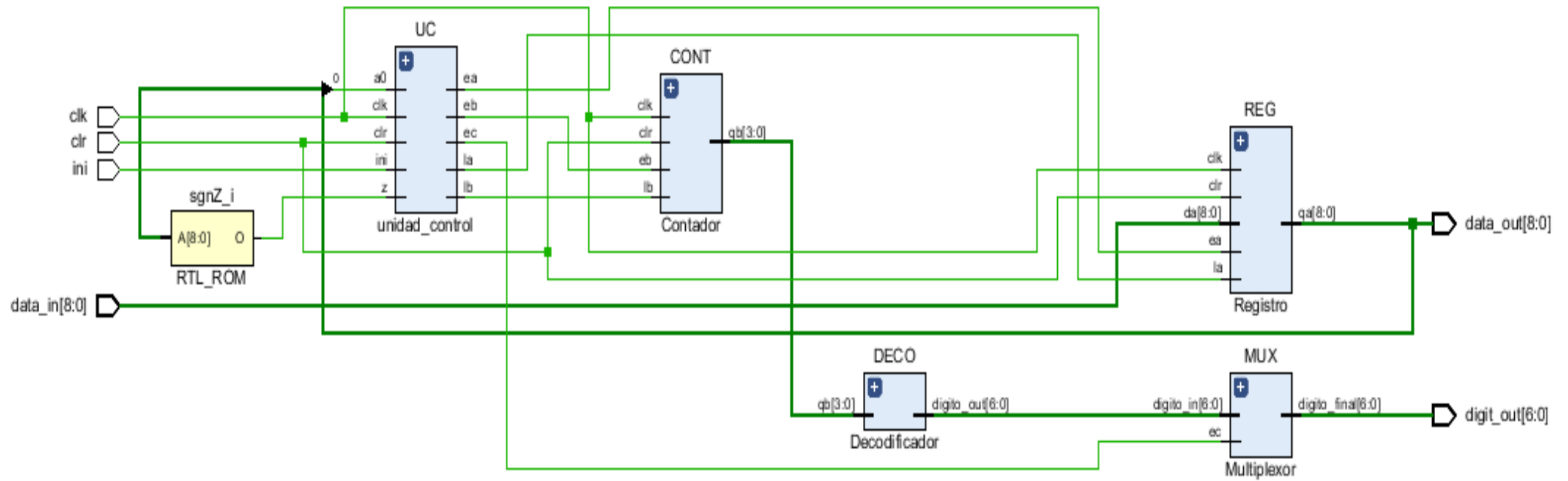


Forma de onda

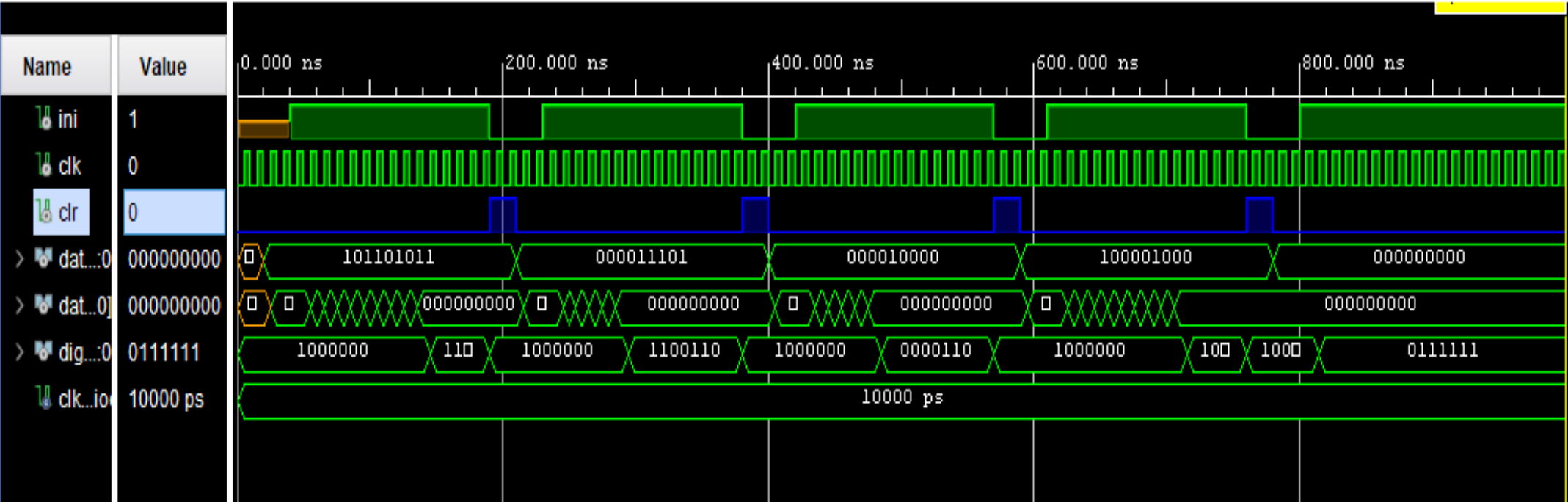


Simulación a

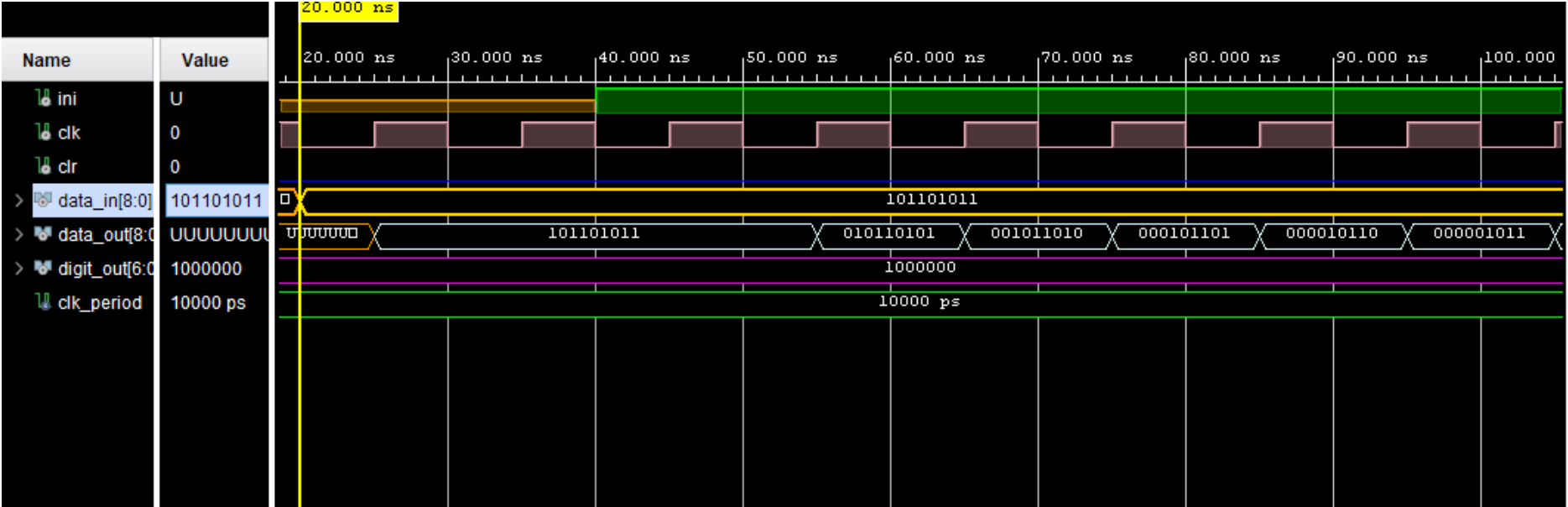


Simulación b

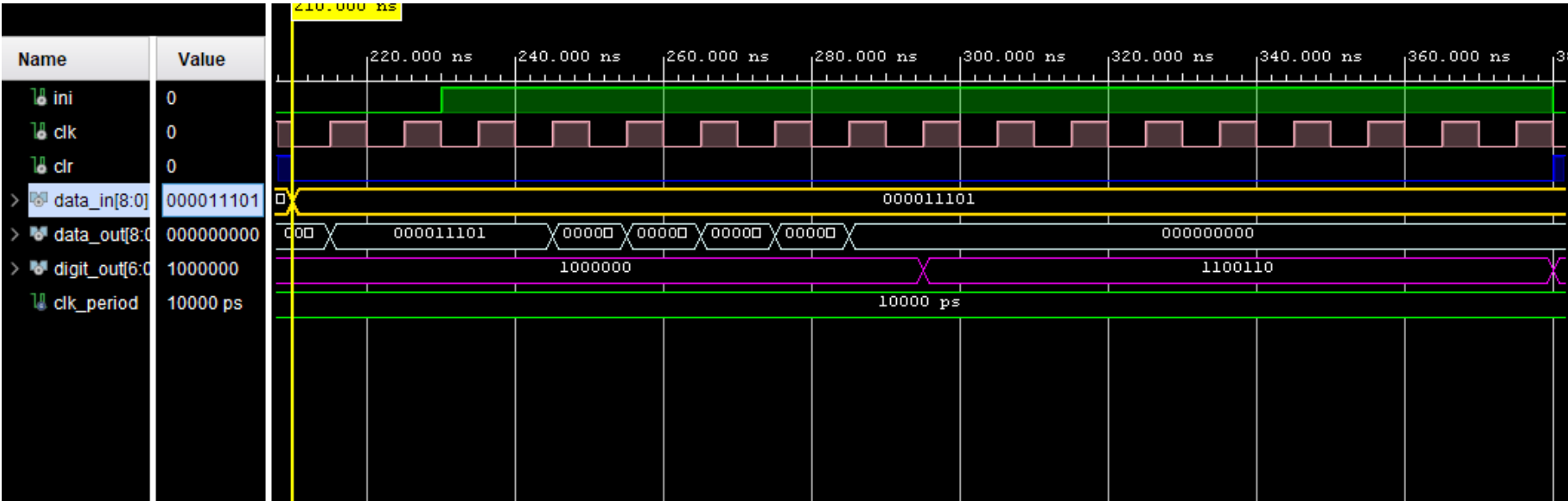

Simulación c

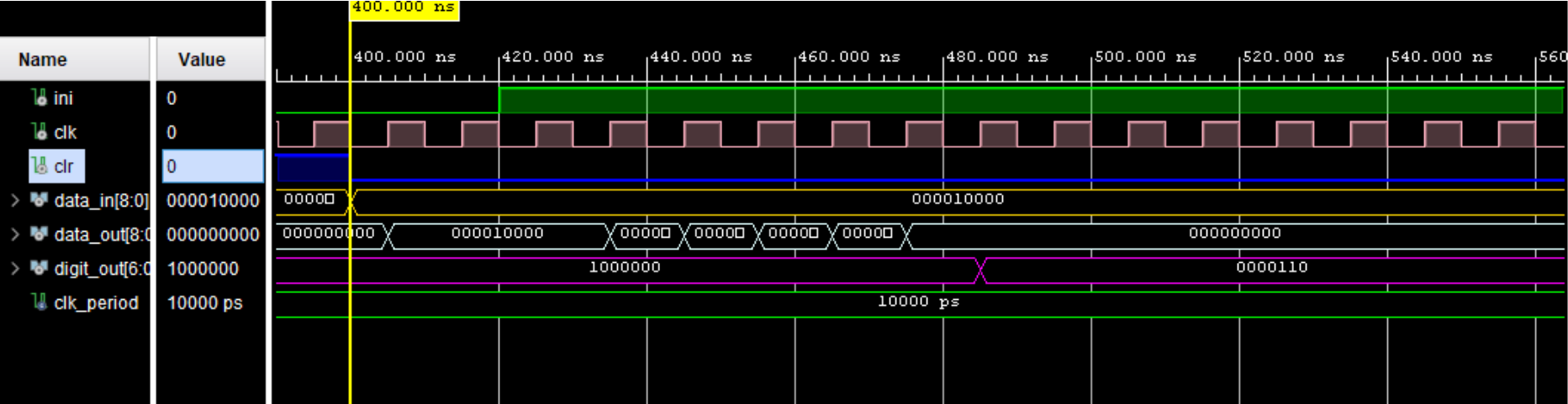

Simulación d

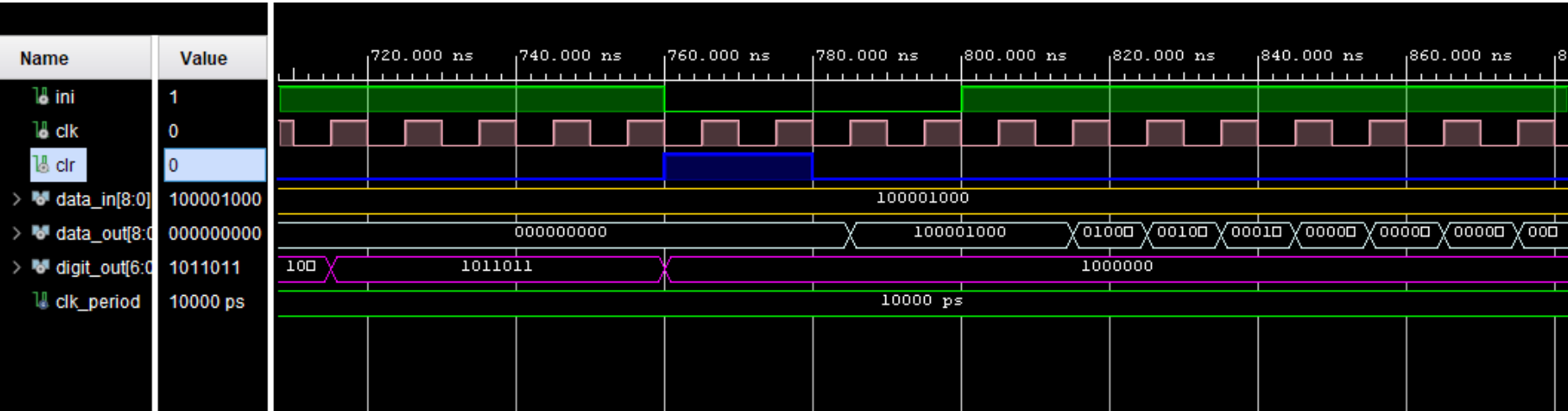

Simulación e

