

## Práctica 4

### Código de implementación:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity sumador4b is
    Port ( a,b : in STD_LOGIC_VECTOR (3 downto 0);
          sel : in STD_LOGIC;
          S : out STD_LOGIC_VECTOR (3 downto 0);
          cout : out STD_LOGIC);
end sumador4b;
architecture Behavioral of sumador4b is
    signal eb: std_logic_vector(3 downto 0);
    signal c: std_logic_vector(4 downto 0);
    begin
        c(0) <= sel;
        cicle : for i in 0 to 3 generate
            eb(i) <= b(i) xor c(0);
            S(i) <= a(i) xor eb(i) xor c(i);
            c(i+1) <= (a(i) and eb(i)) or (a(i) and c(i)) or (eb(i) and c(i));
        end generate;
        cout <= c(4);
    end Behavioral;
```

## Código test-bench:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;


entity sumadorTB is
-- Port ( );
end sumadorTB;

architecture Behavioral of sumadorTB is
component sumador4b is
    Port ( a,b : in STD_LOGIC_VECTOR (3 downto 0);
          sel : in STD_LOGIC;
          S : out STD_LOGIC_VECTOR (3 downto 0);
          cout : out STD_LOGIC);
end component;


signal a,b : STD_LOGIC_VECTOR (3 downto 0);
signal sel : STD_LOGIC;
signal S : STD_LOGIC_VECTOR (3 downto 0);
signal cout : STD_LOGIC;

begin
unidad1: sumador4b
    Port map(
        a => a,
        b => b,
        sel => sel,
        S => S,
        cout => cout
    );
process
begin
    a <= "valor inicial";
    b <= "valor inicial";
    sel <= 'operador (0=+ / 1=-)';
    wait for 20 ns; --espera este tiempo antes de ir
                    --a otra operación
    sel <= 'operador (0=+ / 1=-)';
    a <= "valor nuevo";
    b <= "valor nuevo";
    wait;
end process;
end Behavioral;
```


Diagrama RTL:

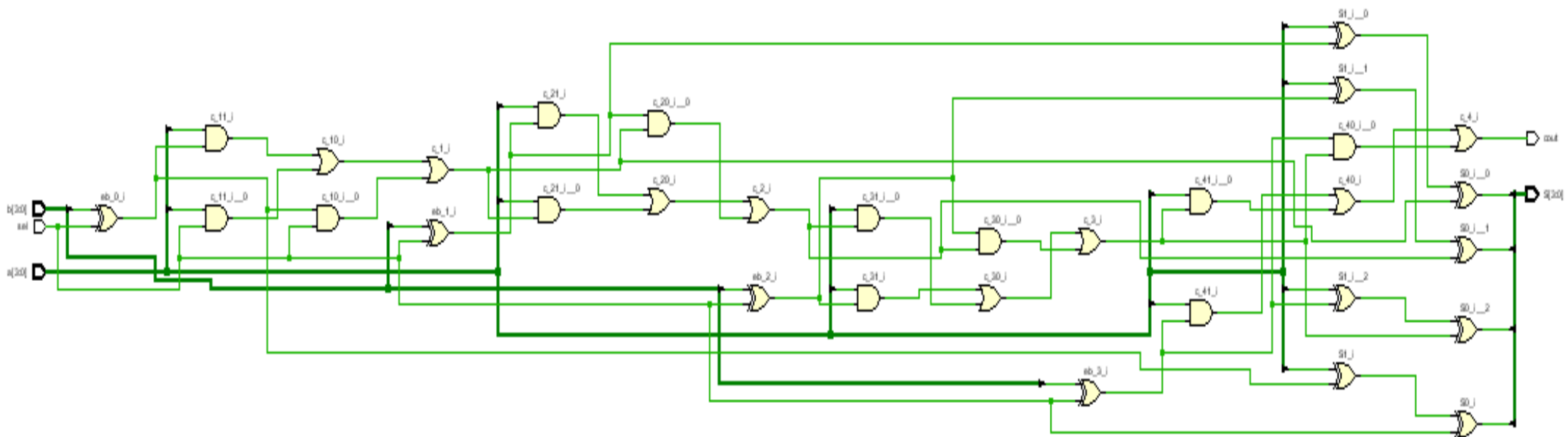

## Diagrama Lógico:

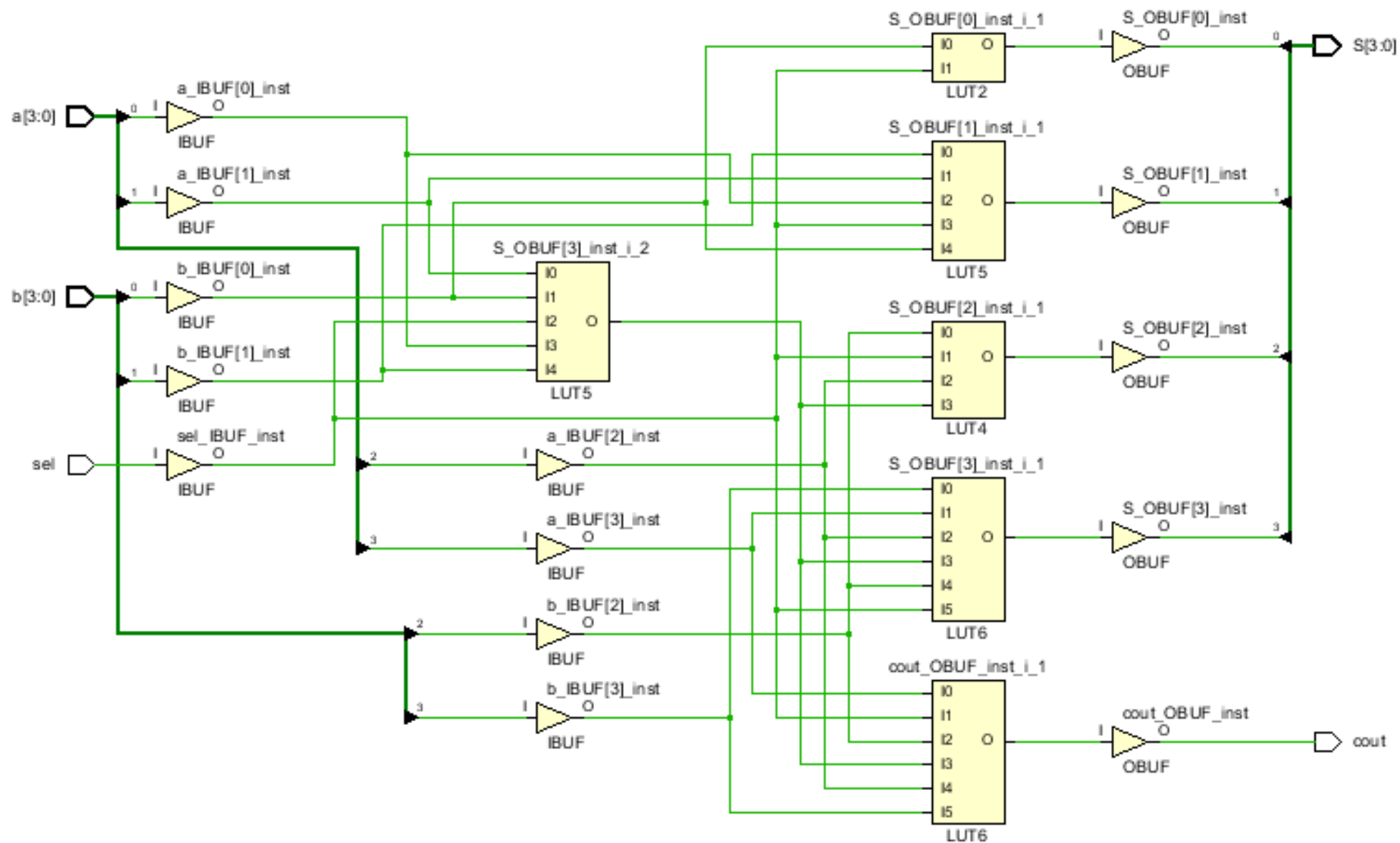

Forma de onda:

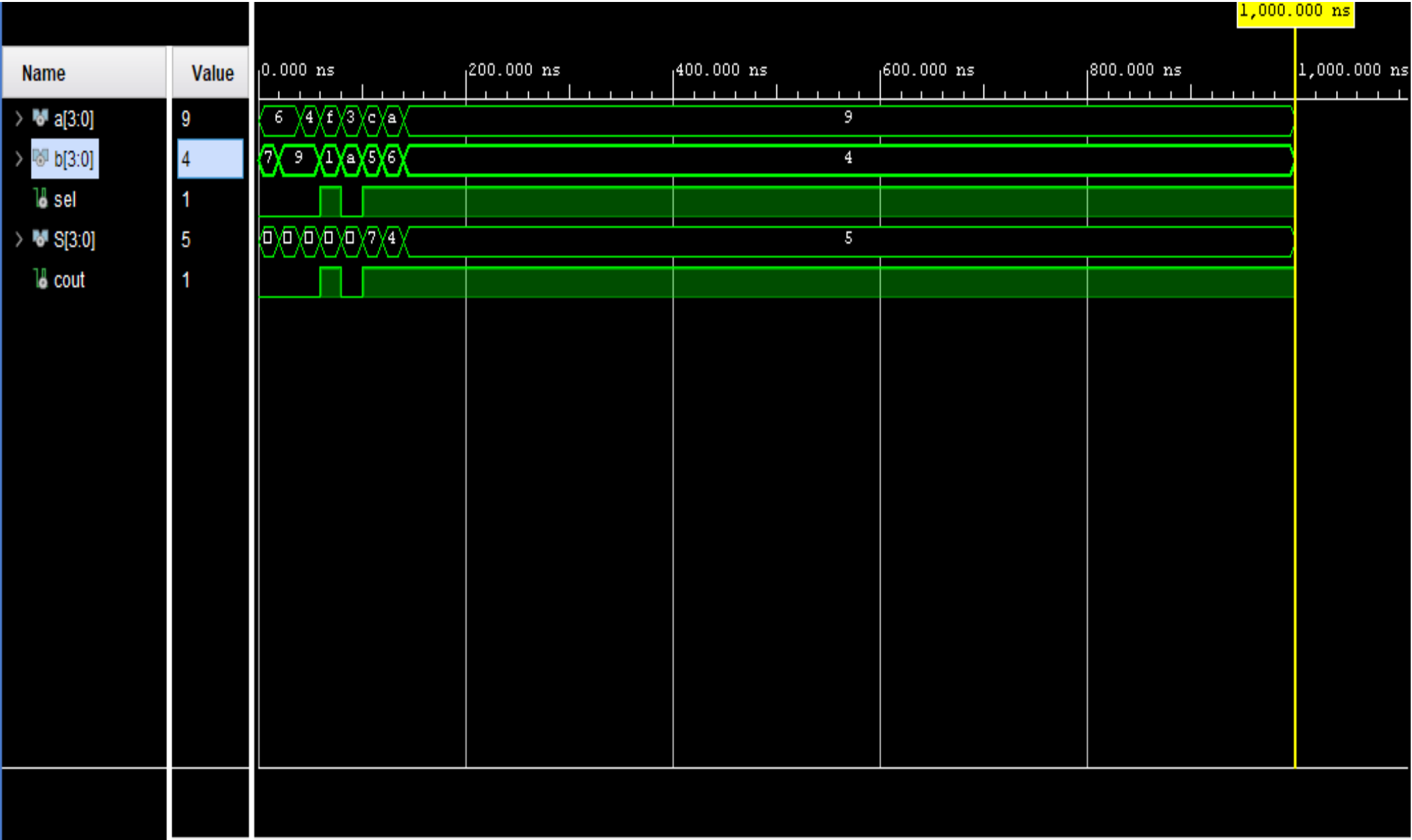

**Tabla de resultados:**

<b>Operación</b>	<b>A</b>	<b>B</b>	<b>S</b>	<b>Cout</b>
<b>Suma</b>	6	7	13	0
<b>Suma</b>	6	9	15	0
<b>Suma</b>	4	9	13	0
<b>Resta</b>	15	1	14	1
<b>Suma</b>	3	10	13	0
<b>Resta</b>	12	5	7	1
<b>Resta</b>	14	8	6	1
<b>Resta</b>	10	6	4	1
<b>Resta</b>	9	4	5	1